

# Design of Embedded Hardware and Firmware

***"System On Programmable Chip"***  
***Programmable interface design***  
*GPIO exemple*

Andres Upegui, René Beuchat

Laboratoire de Systèmes Numériques  
hepia/HES-SO  
4, rue de la Prairie, CH-1202 Genève

*Andres.uegui@hesge.ch*

# Goal


Example of a development methodology of a programmable parallel port interface

**The objective here is to design an interface for an Avalon bus as a slave module.**

The main characteristics of the module are:

- ➔ Bidirectional Port,
- ➔ Programmable Direction for each bit
- ➔ Special features for modifying the port bits

# Typical SOPC

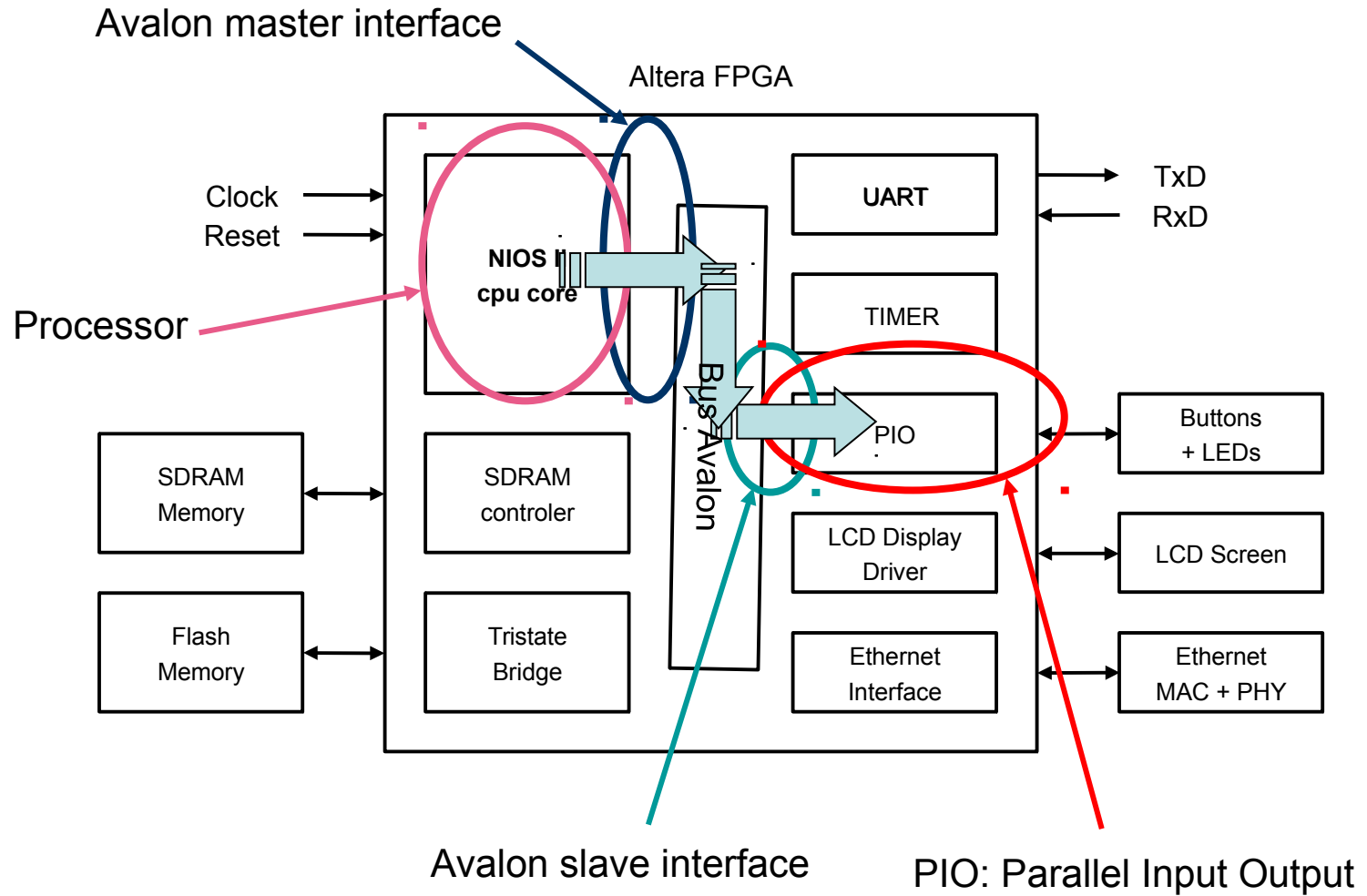

# Parallel Port Interface (1)

- 8 bits bidirectional Port,
  - Each pin can be specified as input or output
  - The direction is specified in **RegDir**, (0 : input, 1 : output)
  - The direction can be read back
- The state of the port at the pin level can be read in : **RegPin**


# Parallel Port Interface (2)

- The state value is stored in a register:  
**RegPort** → Port Register
- 3 possible ways to modify register value :
  1. **RegPort** : Direct memorized value : '0' or '1'
  2. **RegSet** : The bits specified at '1' level during the write cycle at this address, are saved as '1' in the register, the others bits are not changed
  3. **RegClr** : The bits specified at '1' level during the write cycle at this address, are saved as '0' in the register, the others bits are not changed
- This register can be read back

# Programmable interface design : Methodology

- Identify inputs-outputs of the interface (entity)
- Define a register model.
  - The register model is the interface between hardware and software.
  - Typically there are **control, status and data** registers.
  - For the software programmer the interface must remain as simple to use as possible.
  - Try to avoid unnecessary hardware complexity.
- Create your interface architecture:
  - From registers generate outputs.
  - From inputs write on registers.
  - Other registers may also store system state

# Parallel Port Module on Avalon : I/O

 


# I/O Addresses in the module: register model


Adresses in the module	Write Registers	DataWrite [7..0]	Read Registers	DataRead [7..0]
0	RegDir	→ iRegDir	RegDir	iRegDir →
1	-	Don't care	RegPin	ParPort →
2	RegPort	→ iRegPort	RegPort	iRegPort →
3	RegSet	→ iRegPort	-	0x00
4	RegClr	→ iRegPort	-	0x00
5	-	Don't care	-	0x00
6	-	Don't care	-	0x00
7	-	Don't care	-	0x00



# Parallel Port Module on Avalon

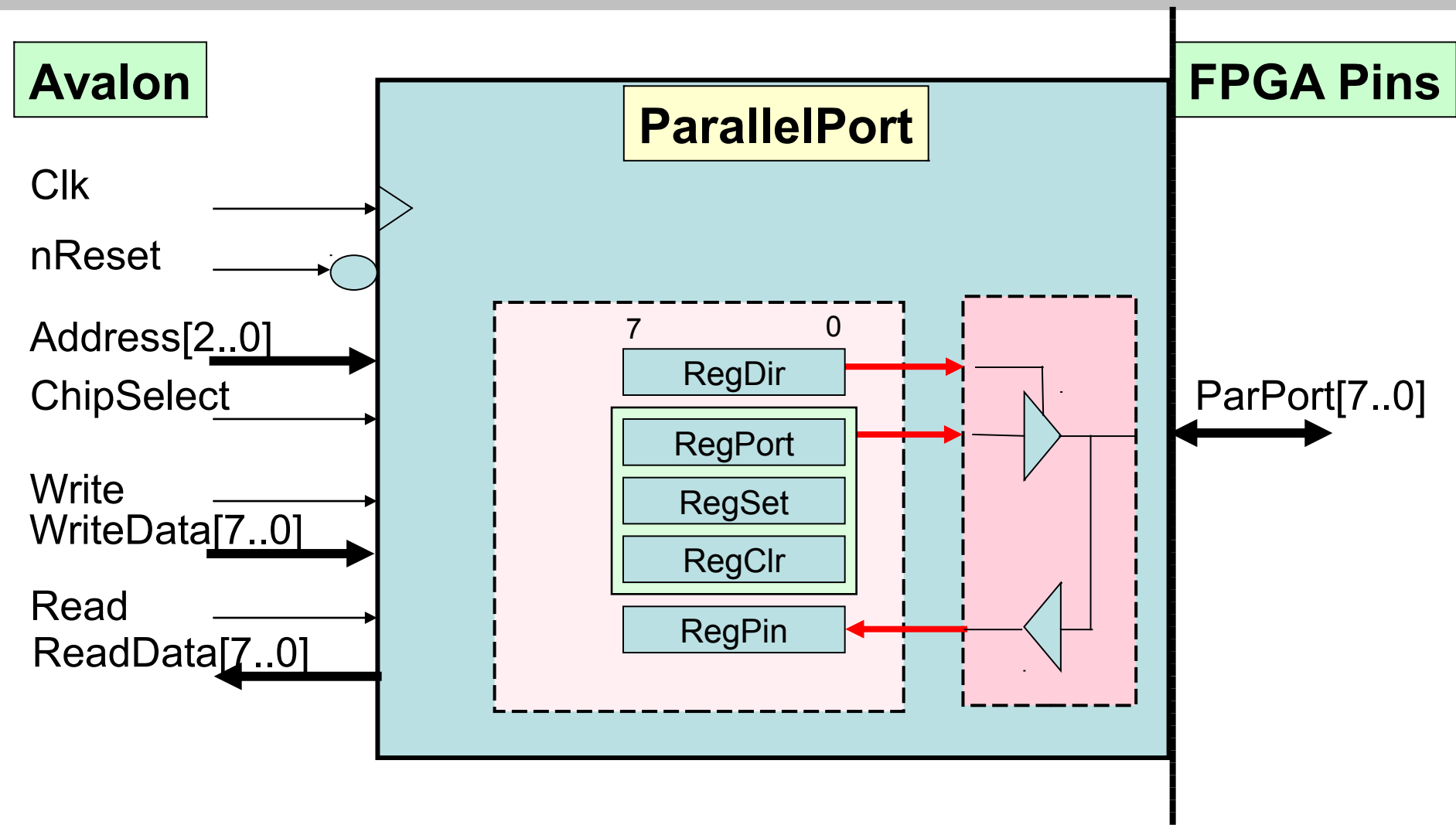
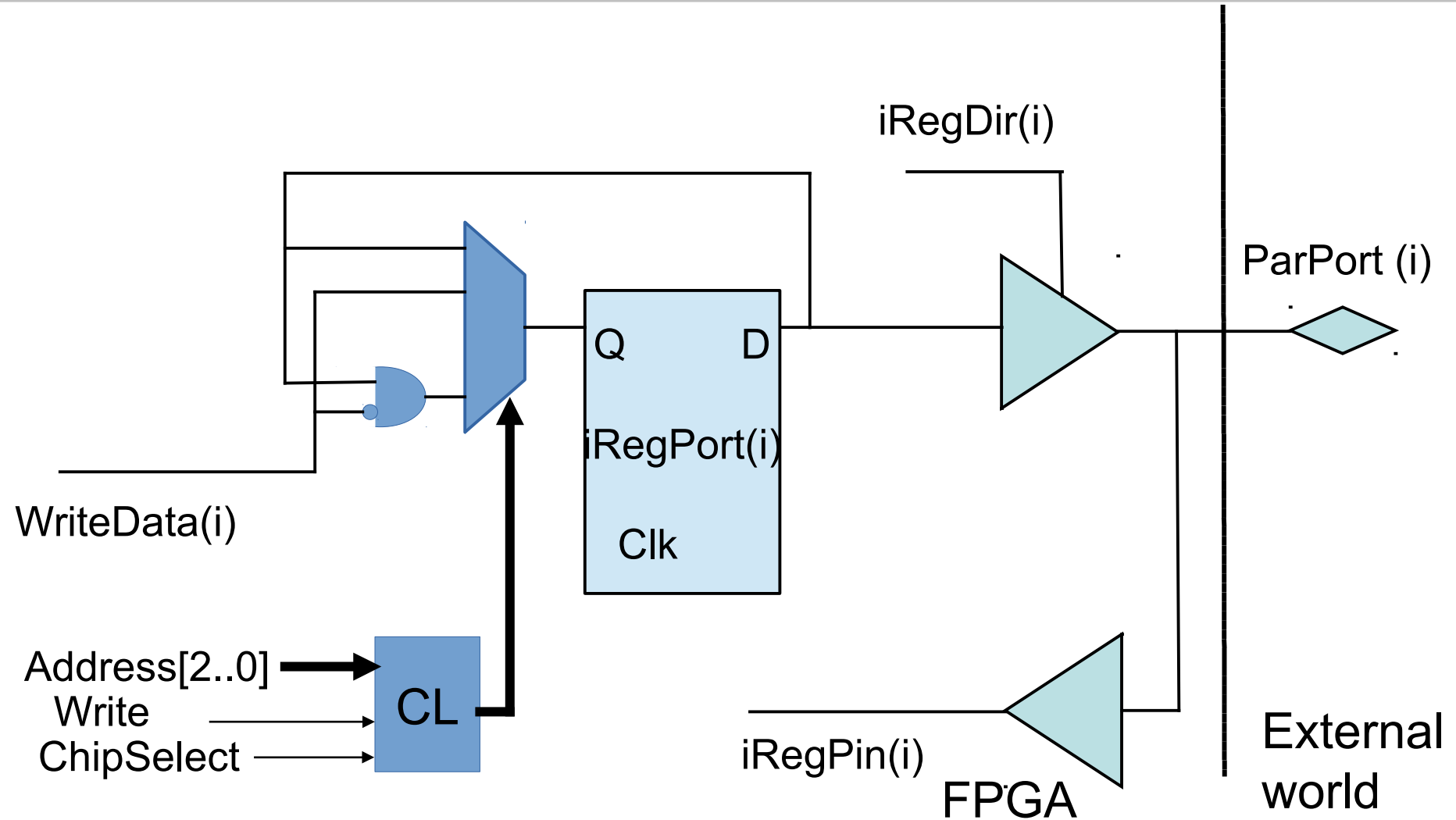
# Parallel Port Module : from Registers to outputs



# Entity

```
ENTITY ParallelPort IS
  PORT (
    -- Avalon interfaces signals
    Clk : IN      std_logic;
    nReset : IN    std_logic;

    Address : IN    std_logic_vector (2 DOWNT0 0);
    ChipSelect : IN  std_logic;

    Read : IN      std_logic;
    Write : IN      std_logic;

    ReadData : OUT  std_logic_vector (7 DOWNT0 0);
    WriteData : IN   std_logic_vector (7 DOWNT0 0);

    -- Parallel Port external interface
    ParPort : INOUT std_logic_vector (7 DOWNT0 0)
  );
End ParallelPort;
```

# Architecture: Internal signals

-- signals for register access

```
iRegDir    : std_logic_vector (7 DOWNTO 0);  
iRegPort: std_logic_vector (7 DOWNTO 0);  
iRegPin    : std_logic_vector (7 DOWNTO 0);
```

# ParallelPort Architecture, registers access (write)

```
ARCHITECTURE comp OF ParallelPort IS
```

```
... SIGNAL ...
```

```
BEGIN
```

```
    process(Clk, nReset)
```

```
    begin
```

```
        if nReset = '0' then
```

```
            iRegDir <= (others => '0');           -- Input by default
```

```
            ...
```

```
        elsif rising_edge(Clk) then
```

```
            if ChipSelect = '1' and Write = '1' then -- Write cycle
```

```
                case Address(2 downto 0) is
```

```
                    when "000" => iRegDir <= WriteData ;
```

```
                    when "010" => iRegPort <= WriteData;
```

```
                    when "011" => iRegPort <= iRegPort OR WriteData;
```

```
                    when "100" => iRegPort <= iRegPort AND NOT WriteData;
```

```
                    when others => null;
```

```
                end case;
```

```
            end if;
```

```
        end if;
```

```
    end process pRegWr;
```

# ParallelPort Architecture, registers access (read)

-- Read from registers with wait 0

```
ReadData <=      iRegDir  when Address= "000" else  
                 iRegPin  when Address= "001" else  
                 iRegPort when Address= "010" else  
                 "00000000";
```

Partially ok... because:

# ParallelPort Architecture, registers access (read)

-- Read Process from registers with wait 1

```
pRegRd:
  process (Clk)
  begin
    if rising_edge(Clk) then
      ReadData <= (others => '0');           -- default value
      if ChipSelect = '1' and Read = '1' then -- Read cycle
        case Address(2 downto 0) is
          when "000" => ReadData <= iRegDir ;
          when "001" => ReadData <= iRegPin;
          when "010" => ReadData <= iRegPort;
          when others => null;
        end case;
      end if;
    end if;
  end process pRegRd;
```

# ParallelPort Architecture, external interface

```
-- Parallel Port output value
pPort:
  process(iRegDir, iRegPort)
  begin
    for i in 0 to 7 loop
      if iRegDir(i) = '1' then
        ParPort(i) <= iRegPort(i);
      else
        ParPort(i) <= 'Z';
      end if;
    end loop;
  end process pPort;

-- Parallel Port Input value
  iRegPin <= ParPort;

END comp;
```

